University of Tripoli

Faculty of Engineering

Electrical & Electronic Engineering Department


Ind Exam

EE463

Time: 1:30 hr

Fall 2017

16/12/2017

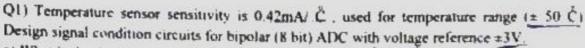


- a) What is the digital output of ADC at the temperature 31 C, -20 C
- b) What is the temperature when the digital output is B6H. [10 pts]

Q2) Design the signal conditioning circuits to connect the sensor to 8 bit ADC with voltage reference (0-10V), where: sensor output range (-100 - +100 mV) with frequency 25Hz. Noise signal 20mV with frequency 260Hz, and using filter that Attenuate the noise signal to 29% of its value, and taking in account the effect of the filter on the sensor signal. [10 pts]

Q3) Using pressure sensor which sensitivity is 2.3mV/bar, and temperature sensor which sensitivity is 100//C and its value at zero $C = 300\Omega$. Design circuit which open Valve when the pressure is more than 15bar, and operate heater when temperature is less than 20 C, and operate Red LED when both of them are $ON_{-}(10\text{ pts})$

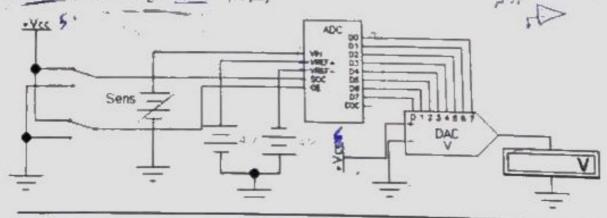Q4) What is the digital value of the ADC output and what is the analog value of DAC output at the temperature 23 C, and -30 C. Where sensor sensitivity=15mV/C, sensor output at 0 C=100mV, sensor range=±50 C [10 pts]



241 12 64 12 14 8 42 1

Good Luck (Zcyad)

Fall 2017

2nf Exam

Q3- Pressure Sensor sensitivity is $2.3 \frac{mv}{boar}$ Temp " " is $10 \frac{\Omega}{C^{\circ}}$ @ o'c = 300.2

* Open Value when P>15bar.

* operate heater " T< 20°c,

* Red led when both ON:

- 15 bor x 213 mu = 34.5 mu

- (20°CX 100) +300 2 = 500 1